

## Half\_adder circuit

May 25, 2022

```
[8]: import numpy as np


# Importing standard Qiskit libraries
from qiskit import QuantumCircuit, transpile, Aer, IBMQ
from qiskit.tools.jupyter import *
from qiskit.visualization import *
from ibm_quantum_widgets import *
from qiskit.providers.aer import QasmSimulator

# Loading your IBM Quantum account(s)
provider = IBMQ.load_account()
```

ibmqfactory.load\_account:WARNING:2022-05-25 11:40:01,657: Credentials are already in use. The existing account in the session will be replaced.


```
[17]: #Designing the half adder circuit for addition of bits
qc = QuantumCircuit(4, 2) #(4,2) creates 4 qubits and 2 cbits, cbits implies
    ↳ classical bits
qc.cx(0,2)
qc.cx(1,2)
qc.ccx(0,1,3)
display(qc.draw())      # display a drawing of the circuit
 
#This circuit adds qubits q0 and q1 and output the result in qubits q2 and q3
    ↳ which will be measured into cbits c1 and c2 as c1 c2
#E.g. q0 + q1 = 1+0 implies c1 c2 = 01 and q0 + q1 = 1+1 implies c1 c2 = 10
#In classical sense, c2 is the half adder sum, and c1 is the carried over sum
# (Note: measurement is not shown in this design)
```



```
[10]: #TESTING THE HALF-ADDER CIRCUIT
test_qc = QuantumCircuit(4, 2)
#First, the circuit should encode an input (here '00' which is 0+0)
#By default, qc(0) and qc(1) are in the states zero |0> , so we need do nothing
    ↳ on them
# Next is to carry out the adder circuit created
test_qc.cx(0,2)
test_qc.cx(1,2)
test_qc.ccx(0,1,3)
# Finally, we will measure the bottom two qubits,q2 and q3 to extract the output
test_qc.measure(2,0) #this measures the 3rd qubit q2, and records it in the 1st
    ↳ cbit c1
test_qc.measure(3,1) #this measures the 4th qubit q3, and records it in the 2nd
    ↳ cbit c2
test_qc.draw()
```

[10]:

 


```
[11]: from qiskit.providers.aer import AerSimulator
sim = AerSimulator() # make new simulator object
job = sim.run(test_qc) # runs the experiment
result = job.result() # get the results
result.get_counts() # interpret the results as a "counts" dictionary
```

```
[11]: {'00': 1024}
```

```
[15]: #In the above we can see that the result '00' was measured 1024 times, and we
      ↪ didn't measure any other result. This is as expected.
      #Now to the next addition, the circuit should encode an input (here '01' which
      ↪ is 0+1)
test1_qc = QuantumCircuit(4, 2)
#By default, qc(0) and qc(1) are in the states zero|0> , so we need do nothing
      ↪ on qc(0) but need to flip qc(1)
test1_qc.x(1) #flips qubit q1 from |0> to |1>
# Next is to carry out the adder circuit created
test1_qc.cx(0,2)
test1_qc.cx(1,2)
test1_qc.ccx(0,1,3)
##Finally, we will measure q2 and q3 to extract the output
test1_qc.measure(2,0) #this measures q2 and records it in c1
test1_qc.measure(3,1) #this measures q3 and records it in c2
test1_qc.draw()
```

```
[15]:
```

 


```
[16]: job1 = sim.run(test1_qc)  # runs the experiment
      result1 = job1.result()  # get the results
      result1.get_counts()     # interpret the results as a "counts" dictionary
```

```
[16]: {'01': 1024}
```

```
[18]: #In the above we can see that the result '01' was measured 1024 times, and we
      ↪ didn't measure any other result. This is as expected.
      #Now to the next addition, the circuit should encode an input (here '10' which
      ↪ is 1+0)
      test2_qc = QuantumCircuit(4, 2)
      #By default, qc(0) and qc(1) are in the states zero|0> , so we need do nothing
      ↪ on qc(1) but need to flip qc(0)
      test2_qc.x(0) #flips qubit q0 from |0> to |1>
      #Next is to carry out the adder circuit created
      test2_qc.cx(0,2)
      test2_qc.cx(1,2)
      test2_qc.ccx(0,1,3)
      #Finally, we will measure q2 and q3 to extract the output
      test2_qc.measure(2,0) #this measures q2 and records it in c1
      test2_qc.measure(3,1) #this measures q3 and records it in c2
      test2_qc.draw()
```

```
[18]:
```

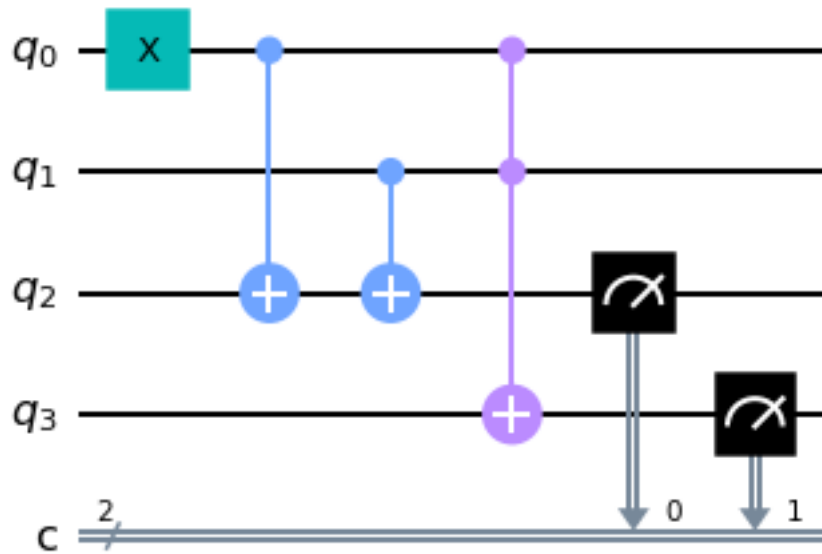


```
[19]: job2 = sim.run(test2_qc)  # runs the experiment
      result2 = job2.result()  # get the results
      result2.get_counts()     # interpret the results as a "counts" dictionary
```

```
[19]: {'01': 1024}
```

```
[20]: #In the above we again can see that the result '01' was measured 1024 times,
      ↪ and we didn't measure any other result. This is as expected.
      #Now to the next addition, the circuit should encode an input (here '11' which
      ↪ is 1+1)
      test3_qc = QuantumCircuit(4, 2)
      #By default, qc(0) and qc(1) are in the states zero|0> , so we need to flip them
      test3_qc.x(0) #flips qubit q0 from |0> to |1>
      test3_qc.x(1) #flips q1 from |0> to |1>
      #Next is to carry out the adder circuit created
      test3_qc.cx(0,2)
      test3_qc.cx(1,2)
      test3_qc.ccx(0,1,3)
      #Finally, we will measure q2 and q3 to extract the output
      test3_qc.measure(2,0) #this measures q2 and records it in c1
      test3_qc.measure(3,1) #this measures q3 and records it in c2
      test3_qc.draw()
```

```
[20]:
```

 

```
[21]: job3 = sim.run(test3_qc) # runs the experiment
      result3 = job3.result() # get the results
      result3.get_counts() # interpret the results as a "counts" dictionary
```

```
[21]: {'10': 1024}
```

```
[ ]: #In the above we again can see that the result '10' was measured 1024 times,
      ↪and we didn't measure any other result.
      #The half adder contains everything needed for addition.
      #With the NOT qc.x(arg), CNOT qc.cx(arg), and Toffoli gates qc.ccx(arg), we can
      ↪create programs that add any set of numbers of any size.

      #Davikky, 5/25/2022
```